

# Placement preparation VERILOG Assignment (7<sup>th</sup> AUGUST)

## SYSTEM-TASKS & COMPILER DIRECTIVES Assignment

### Snippet #1: -

```
module practice;

integer a,b,c;

reg [2:0] x,y,z;

integer i;

initial begin

a = 10;

b =17;

c = 34;

for(i=0;i<8;i=i+1) begin

x <= i;

#5;

y <= x+1'b1;

#5;

z <= x+y;

#5;

end

$strobe("$STROBE OUTPUT__Value of x = %0d, y=%0d, z=%0d",x,y,z);

$display("$DISPLAY OUTPUT__Value of x = %0d, y=%0d, z=%0d",x,y,z);

end

initial

$monitor("$MONITOR OUTPUT__Value of x = %0d, y=%0d, z=%0d",x,y,z);

endmodule
```

### Output Snippet #1:-

Time resolution is 1 ps

\$MONITOR OUTPUT\_\_Value of x = 0, y=x, z=x

\$MONITOR OUTPUT\_\_Value of x = 0, y=1, z=x

\$MONITOR OUTPUT\_\_Value of x = 0, y=1, z=1

\$MONITOR OUTPUT\_\_Value of x = 1, y=1, z=1

\$MONITOR OUTPUT\_\_Value of x = 1, y=2, z=1

\$MONITOR OUTPUT\_\_Value of x = 1, y=2, z=3

\$MONITOR OUTPUT\_\_Value of x = 2, y=2, z=3

\$MONITOR OUTPUT\_\_Value of x = 2, y=3, z=3

\$MONITOR OUTPUT\_\_Value of x = 2, y=3, z=5

\$MONITOR OUTPUT\_\_Value of x = 3, y=3, z=5

\$MONITOR OUTPUT\_\_Value of x = 3, y=4, z=5

\$MONITOR OUTPUT\_\_Value of x = 3, y=4, z=7

\$MONITOR OUTPUT\_\_Value of x = 4, y=4, z=7

\$MONITOR OUTPUT\_\_Value of x = 4, y=5, z=7

\$MONITOR OUTPUT\_\_Value of x = 4, y=5, z=1

\$MONITOR OUTPUT\_\_Value of x = 5, y=5, z=1

\$MONITOR OUTPUT\_\_Value of x = 5, y=6, z=1

\$MONITOR OUTPUT\_\_Value of x = 5, y=6, z=3

\$MONITOR OUTPUT\_\_Value of x = 6, y=6, z=3

\$MONITOR OUTPUT\_\_Value of x = 6, y=7, z=3

\$MONITOR OUTPUT\_\_Value of x = 6, y=7, z=5

\$MONITOR OUTPUT\_\_Value of x = 7, y=7, z=5


\$MONITOR OUTPUT\_\_Value of x = 7, y=0, z=5

\$MONITOR OUTPUT\_\_Value of x = 7, y=0, z=7

\$DISPLAY OUTPUT\_\_Value of x = 7, y=0, z=7

\$STROBE OUTPUT\_\_Value of x = 7, y=0, z=7

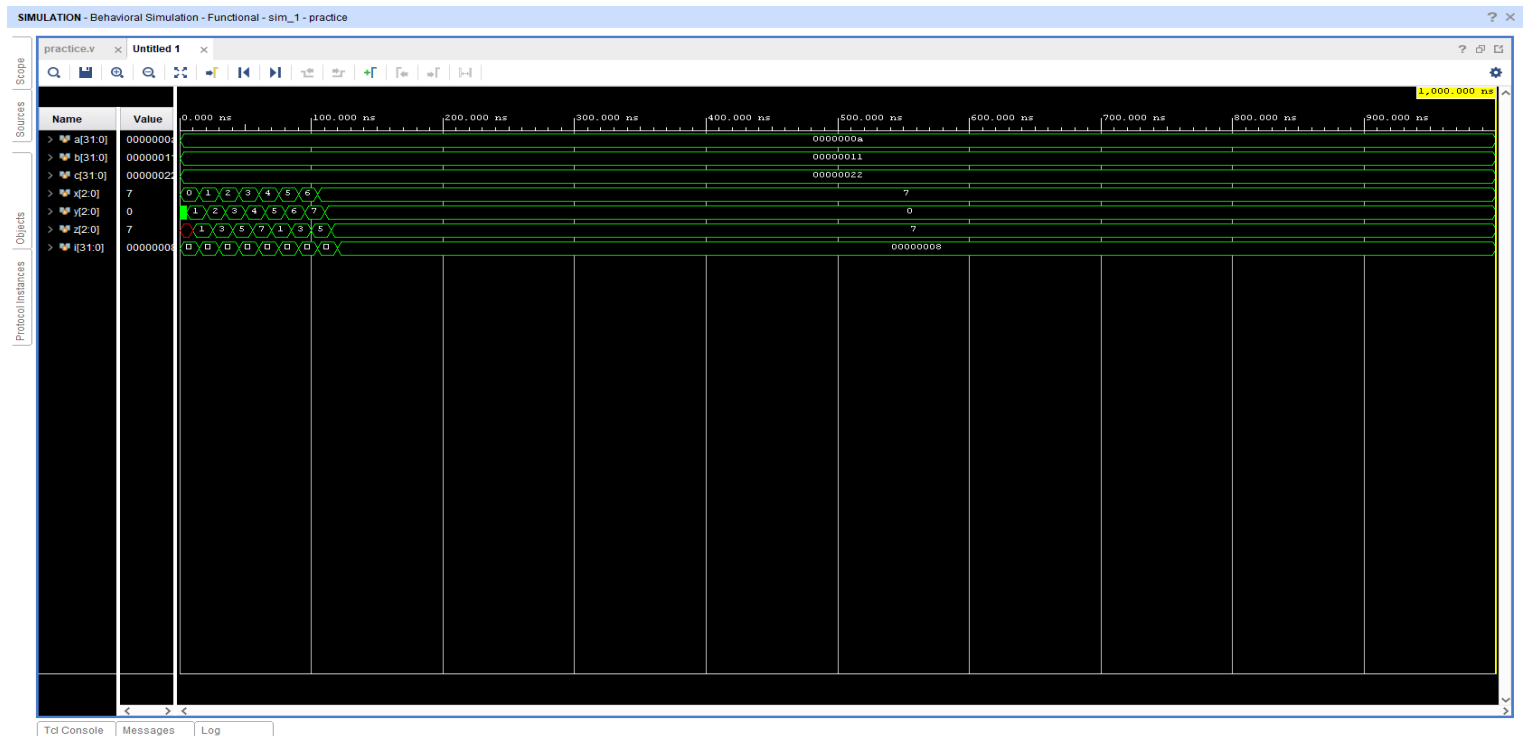relaunch\_sim: Time (s): cpu = 00:00:02 ; elapsed = 00:00:07 . Memory (MB): peak = 875.629 ; gain = 0.



-----#####-----

## Snippet #2: -

module tb;

integer a=0;

integer b = 0;

integer i,j;

time t;

initial begin

for(i=0;i<4;i=i+1) begin

a = a+i;

#0;

\$strobe("Value of a is: %0d",a,\$time);

end

for(j=0;j<4;j=j+1) begin

b = b+j;

#0;

\$display("Value of b is: %0d",b,\$time);

end

```
#100$finish;


end
```

```
endmodule
```

**Output Snippet #2:-**

```
# KERNEL: Value of b is: 0      0
# KERNEL: Value of b is: 1      0
# KERNEL: Value of b is: 3      0
# KERNEL: Value of b is: 6      0
# KERNEL: Value of a is: 6      0
 
# RUNTIME: Info: RUNTIME_0068 design.sv (48): $finish called.
```



-----#####-----

**Snippet #3: -**

```
module prac;

integer i, j;

initial

begin

for(i = 0 ; i < 8; i = i+1)

begin

$display("[$display],Value of i = %d",i);

end

end
```

```

end

initial

begin

for(i = 0 ; i < 8; i = i+1)

begin

$monitor("[$monitor],Value of i = %d",i);

end

end

endmodule

```

### **Output Snippet #3:-**

```

# KERNEL: [$display],Value of i =      0
# KERNEL: [$display],Value of i =      1
# KERNEL: [$display],Value of i =      2
# KERNEL: [$display],Value of i =      3
# KERNEL: [$display],Value of i =      4
# KERNEL: [$display],Value of i =      5
# KERNEL: [$display],Value of i =      6
# KERNEL: [$display],Value of i =      7
# KERNEL: [$display],Value of i =      8
# KERNEL: [$strobe],Value of i =      8
# KERNEL: Simulation has finished.

```

### **Snippet #4: - (DUAL PORT RAM(`define compiler directive))**

**RTL: -**

```

`define width 8

`define depth 16

module dual_ram(we_clk,re_clk,rst,din,we,re,we_addr,re_addr,dout);

input rst,we,re,we_clk,re_clk,we,re;

input [(`width-1):0] din;

input [3:0]we_addr,re_addr;

output reg[3:0]dout;

integer i,j;

```

```
reg[(`width-1):0]mem[(`depth-1):0];
```

```
always@(posedge we_clk)
```

```
begin
```

```
if(rst)
```

```
begin
```

```
for(i=0;i<`depth;i=i+1)
```

```
begin
```

```
mem[i]=0;
```

```
dout=0;
```

```
end
```

```
end
```

```
else
```

```
begin
```

```
mem[we_addr]=din;
```

```
end
```

```
end
```

```
always@(posedge re_clk)
```

```
begin
```

```
if(rst)
```

```
begin
```

```
for(j=0;j<`depth;j=j+1)
```

```
begin
```

```
mem[j]=0;
```

```
dout=0;
```

```
end
```

```
end
```

```
else
```

```
begin
```

```
dout=mem[re_addr];
```

```
end
```

```
end  
endmodule
```

### TESTBENCH: -

```
module dual_ram_tb();  
  
    reg rst,we,re,we_clk,re_clk;  
  
    reg [7:0] din;  
  
    reg [3:0]we_addr,re_addr;  
  
    wire [3:0]dout;  
  
  
    integer i,j,l,o;  
  
    parameter depth=16;  
  
    parameter width=8;  
  
    parameter c1=10;  
  
    reg[(width-1):0]mem[(depth-1):0];  
  
  
    dual_ram DUT(we_clk,re_clk,rst,din,we,re,we_addr,re_addr,dout);  
  
  
    always  
    begin  
        #(c1/2);  
  
        we_clk=1'd1;  
  
        #(c1/2);  
  
        we_clk=1'd0;  
  
    end  
  
  
    always  
    begin  
        #(c1);  
  
        re_clk=1'd1;  
  
        #(c1);  
  
        re_clk=1'd0;
```

```
end
```

```
task initialise;
```

```
begin
```

```
we=0;re=0;
```

```
end
```

```
endtask
```

```
task write(input [3:0]i,input[7:0]j);
```

```
begin
```

```
@(negedge we_clk)
```

```
we=1'b1;
```

```
we_addr=i;
```

```
din=j;
```

```
end
```

```
endtask
```

```
task read(input [3:0]y);
```

```
begin
```

```
@(negedge re_clk)
```

```
re=1'b1;
```

```
re_addr=y;
```

```
end
```

```
endtask
```

```
task reset;
```

```
begin
```

```
#c1
```

```
rst=1'd1;
```

```
#c1
```

```
rst=1'd0;
```

```
end
```

```
endtask
```




```
task delay;  
  
begin  
  
#10;  
  
end  
  
endtask
```

```
initial  
  
begin  
  
reset();  
  
initialise();  
  
delay();  
  
for(l=0;l<16;l=l+1)  
  
write(l,l);  
  
delay();  
  
for(o=0;o<16;o=o+1)  
  
read(o);  
  
delay();  
  
end
```

```
initial  
  
begin  
  
$dumpfile("file.vcd");  
  
$dumpvars();  
  
#2000 $finish;  
  
end
```

```
endmodule
```

**Output Snippet #4:-**

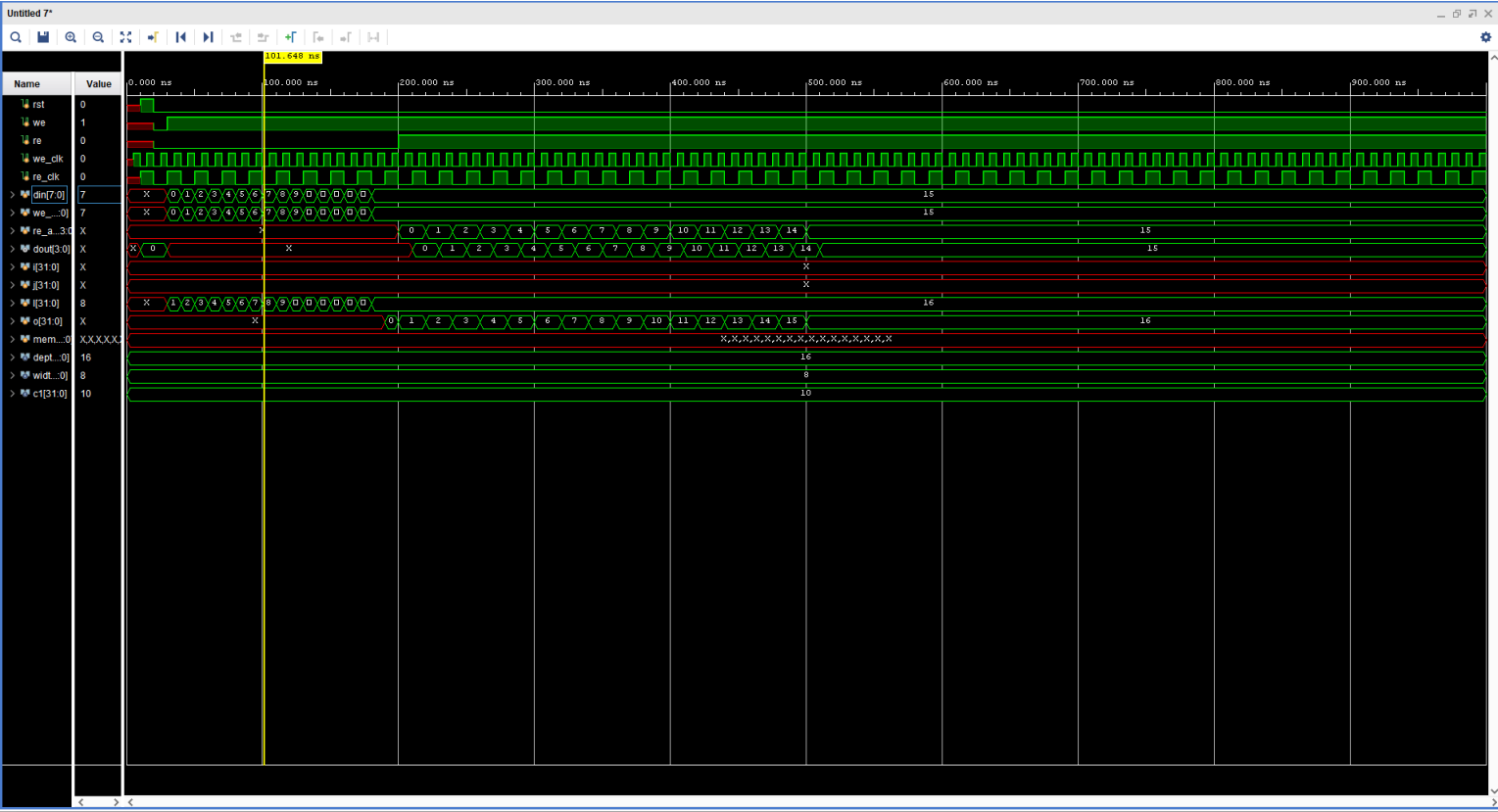

-----#####-----

**Snippet #5: - (JK FLIP FLOP(`include compiler directive))**

RTL: -

#1

```
`include "include.v"

module jk_flip_flop(clk,reset, j,k,q);

input clk,reset,j,k;

output reg q;

always@(posedge clk) begin

if(reset)

q<=0;

else

begin

case({j,k})

`HOLD: q<=q;

`RESET: q<=0;

`SET: q<=1;

`TOGGLE: q<=~q;
```

endcase

end

end

endmodule

**RTL: -**

#2

`define HOLD 0

`define RESET 1

`define SET 2

`define TOGGLE 3

**TESTBENCH: -**

module jk\_flip\_flop\_tb;

reg clk,reset,j,k;

wire q;

jk\_flip\_flop DUT(clk,reset,j,k,q);

always begin

#2 clk = 1'b1;

#2 clk = ~clk;

end

initial begin

@(negedge clk)

reset = 1'b1;

@(negedge clk)

reset = 1'b0;

#2;

{j,k} = 2'b00;


#5;

{j,k} = 2'b01;

#5;

{j,k} = 2'b10;



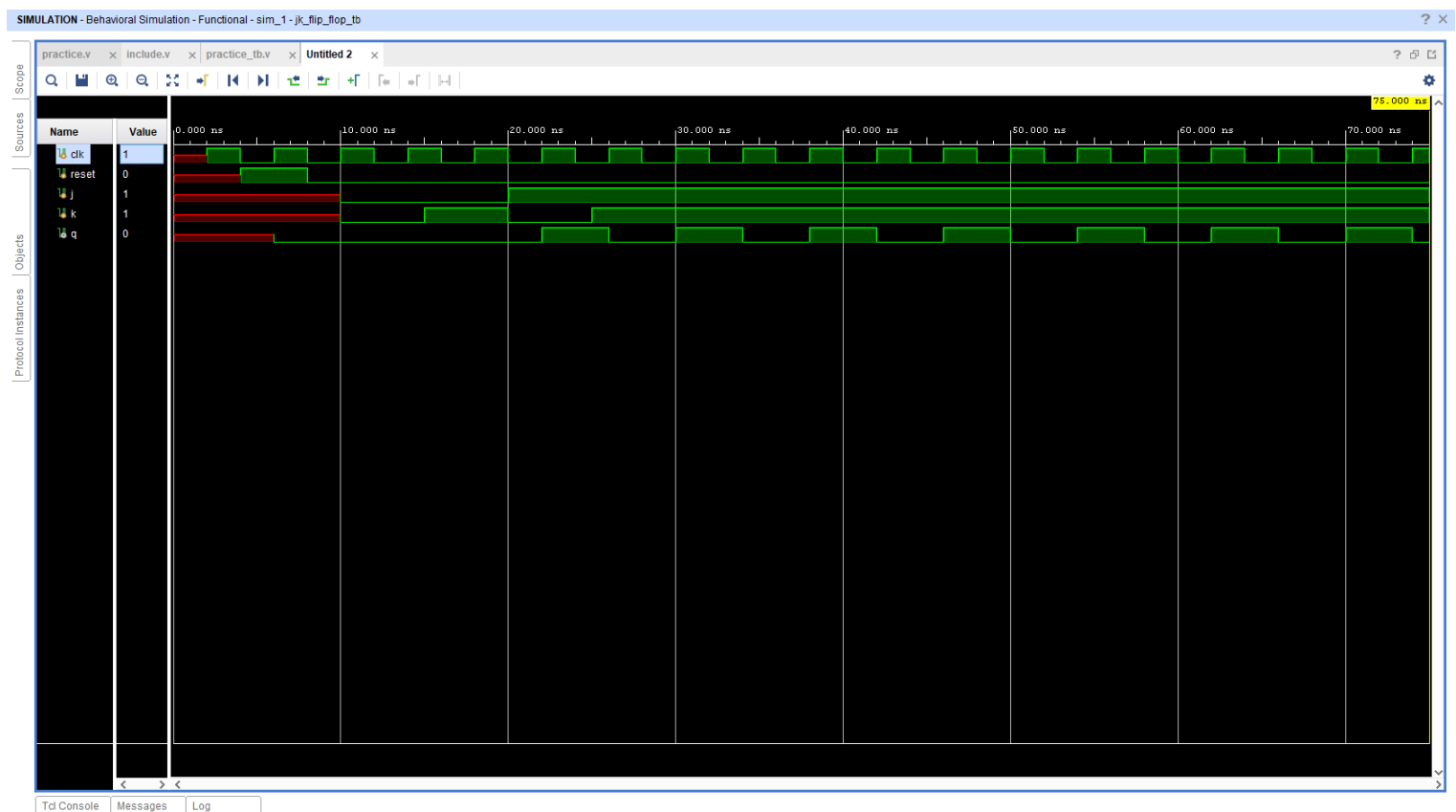

## Snippet #6: - (Dual-Ram RTL (File Operations))

RTL: -

```
module dual_ram(clk,rst,din,we,re,we_addr,re_addr,dout);
```

```
    input clk,we,re,rst;
    input  [3:0]we_addr,re_addr;
    input  [7:0]din;
    output reg [7:0]dout;
    integer i;
    parameter dp=16,wd=8,adrs=4;
    reg[(wd-1):0] mem[(dp-1):0];
```

```
    always@(clk,din,we,re,we_addr,re_addr)
    begin
        if(rst)
            begin
                for(i=0;i<16;i=i+1)
                    mem[i]<=0;
                dout<=0;
            end
```

```
        else
            begin
                if(we)
                    begin
                        mem[we_addr]<=din;
                    end
```

```
            if(re)
```

```

begin
dout<=mem[re_addr];
end
end
end
endmodule

```

## **TESTBENCH: -**

```

module File_Operation;

    reg clk,we,re,rst;
    reg [3:0]we_addr,re_addr;
    reg [7:0]din;
    wire [7:0]dout;
    integer l,chanel_1;
    parameter cycle=10;

    dual_ram DUT(clk,rst,din,we,re,we_addr,re_addr,dout);

    always
    begin
        #(cycle/2);
        clk=1'b1;
        #(cycle/2)
        clk=1'b0;
    end

    task reset();
    begin
        @(negedge clk)
        rst=1'b1;
        @(negedge clk)
        rst=1'b0;
    end
    endtask

    initial
    begin
        reset();

        begin
            we=1; re=0;
            @(negedge clk)
            begin
                $readmemb("text.txt",DUT.mem);
                chanel_1=$fopen("optext.out");
                for(l=0;l<8;l=l+1)
                $fdisplay(chanel_1,"memory[%d]=%b",l,DUT.mem[l]);
                $fclose(chanel_1);
            end
        end
    end

    initial
    begin
        $dumpfile("file.vcd");


```

```
$dumpvars();  
#2000 $finish;  
end
```


```
endmodule
```
 
### Text file in SIM folder "text.txt"

```
01010101  
11111111  
00000000  
00001111  
11001100  
00110011  
10101010  
11100011
```


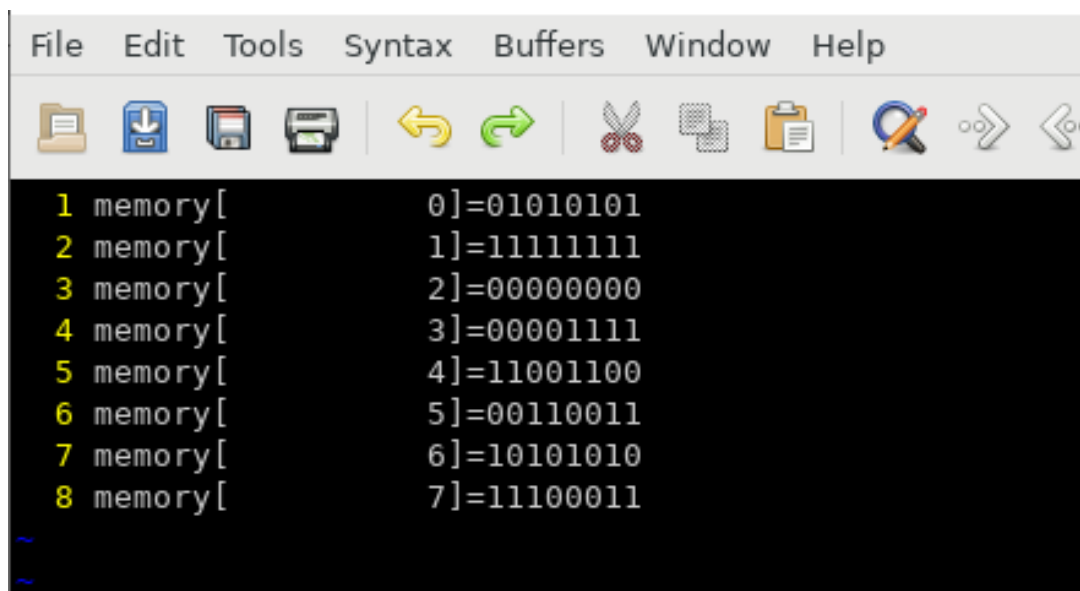
### Output file in SIM folder "optext.out"



## SYNTHESIS CODING STYLES.

### [1]. Combinational Circuit Modelling using always

#### RTL: -

```
module decoder(in,out);

    input [2:0] in;

    output reg [7:0] out;


always @ (in)

begin

out = 0; ///##__if we don't initialize the out value to logic '0', we might get a latch.__###

case (in)

    3'b001 : out = 8'b0000_0001;

    3'b010 : out = 8'b0000_0010;

    3'b011 : out = 8'b0000_0100;

    3'b100 : out = 8'b0000_1000;

    3'b101 : out = 8'b0001_0000;

    3'b110 : out = 8'b0100_0000;

        3'b111 : out = 8'b1000_0000;

endcase

end

endmodule
```

#### TESTBENCH: -

```
module decoder_tb;

reg [2:0] in;

wire [7:0] out;

integer i;
```



```

decoder DUT(in,out);

initial begin

    for(i=0;i<8;i=i+1) begin

        in = i;

        #5;

    end

end

end

initial

    $monitor("For input:%b, Output is:%b",in,out);

endmodule

```

## **OUTPUT: -**

```

# KERNEL: For input:000, Output is:00000000
[-if'out' is not initialized-># KERNEL: For input:000, output is:xxxxxxx]
# KERNEL: For input:001, Output is:00000001
# KERNEL: For input:010, Output is:00000010
# KERNEL: For input:011, Output is:00000100
# KERNEL: For input:100, Output is:00001000
# KERNEL: For input:101, Output is:00010000
# KERNEL: For input:110, Output is:01000000
# KERNEL: For input:111, Output is:10000000
# KERNEL: Simulation has finished. There are no more test vectors to simulate.

```

## **[2]. Combinational Circuit Modelling taking care of sensitivity list and missing case values.**

### **RTL: -**

```

module mux_41 (a, b, c, d, sel, out);

output reg out;

input a, b, c, d;

```

```
input [1:0] sel;

always @(sel or a or b or c or d)

begin
    case (sel)
        2'd0: out = a;
        2'd1: out = b;
        2'd3: out = d;
        default: out = 0;

    endcase
end

endmodule
```

### **TESTBENCH: -**

```
module mux_41_tb;

reg a, b, c, d;
    reg[1:0] sel;

wire out;

integer i;


    mux_41 DUT(a, b, c, d, sel, out);


initial begin

    sel = 0;

    a = 1;

    b = 0;

    c = 1;

    d = 1;

    #5;

    for(i=0;i<4;i=i+1) begin

        sel = i;

        #5;
```

end

end

initial

```
$monitor("For Select input %b, Output is:%b",sel,out);
```

endmodule

### **OUTPUT: -**

**[-Although we didn't consider 'sel' value of '2', it is giving logic '0' at the output for sel=2. This is because we are mentioning the default assignment value in the case.**

**- Also, we have included all the signals in the sensitivity list of the always block to avoid missing any transition for a particular signal.]**

```
# KERNEL: For Select input 00, Output is:1
```

```
# KERNEL: For Select input 01, Output is:0
```

```
# KERNEL: For Select input 10, Output is:0
```

```
# KERNEL: For Select input 11, Output is:1
```

```
# KERNEL: Simulation has finished. There are no more test vectors to simulate.
```

### **[3]. Priority logic Vs. Parallel logic.**

#### **RTL#1: -**

```
module encoder(x,y);
```

```
input[3:0] x;
```

```
output reg[1:0]y;
```

```
always @(x)
```

```
begin : encode
```

```
if (x == 4'b0001) y = 2'b00;
```

```
else if (x == 4'b0010) y = 2'b01;
```

```
else if (x == 4'b0100) y = 2'b10;
```

```
else if (x == 4'b1000) y = 2'b11;
```

```
else y = 2'bxx;
```

```
end
```

```
endmodule
```

### **TESTBENCH#1: -**

```
module encoder_tb;
```

```
reg [3:0] x;
```

```
wire [1:0]y;
```

```
encoder DUV(x,y);
```

```
initial begin
```

```
x = 1;
```

```
#3;
```

```
x = 2;
```

```
#3;
```

```
x = 4;
```

```
#3;
```

```
x = 8;
```

```
#50 $finish;
```

```
end
```

```
initial
```

```
$monitor("for input x:%b, output is:%b",x,y);
```

```
initial
```

```
begin
```

```
$dumpfile("encoder.vcd");
```

```
$dumpvars();
```

```
end
```

```
endmodule
```

### **OUTPUT#1: -**

**[This style of cascaded logic may adversely affect the performance of the circuit.]**

```
# KERNEL: for input x:0001, output is:00
```


```
# KERNEL: for input x:0010, output is:01
```

```
# KERNEL: for input x:0100, output is:10
```

```
# KERNEL: for input x:1000, output is:11
```

# RUNTIME: Info: RUNTIME\_0068 testbench.sv (18): \$finish called.

# KERNEL: Time: 59 ns

 

**RTL#2: -**

```
module encoder(x,y);
```

```
input[3:0] x;
```

```
output reg[1:0]y;
```

```
always @(*)begin
```

```
    y = 0;
```

```
    case(x)
```

```
        4'b0001: y = 2'b00;
```

```
        4'b0010: y = 2'b01;
```

```
        4'b0100: y = 2'b10;
```

```
        4'b1000: y = 2'b11;
```

```
        default: y = 2'bxx;
```

```
    endcase
```

```
end
```

```
endmodule
```

**TESTBENCH#2: -**

```
module encoder_tb;
```

```
    reg [3:0] x;
```

```
    wire [1:0]y;
```

```
    encoder DUV(x,y);
```

```
    initial begin
```

```
x = 1;
#3;
x = 2;
#3;
x = 4;
#3;
x = 8;

#50 $finish;

end

initial
$monitor("for input x:%b, output is:%b",x,y);


initial
begin
$dumpfile("encoder.vcd");
$dumpvars();
end

endmodule
```

## **OUTPUT#2: -**

 **[To avoid “priority logic” use the case construct]**

```
# KERNEL: for input x:0001, output is:00
# KERNEL: for input x:0010, output is:01
# KERNEL: for input x:0100, output is:10
# KERNEL: for input x:1000, output is:11
# RUNTIME: Info: RUNTIME_0068 testbench.sv (18): $finish called.
```



## [4]. Avoiding Latch formation.

### RTL: -

```
module dff(q, d, clk, set, rst);
```

```
input d, clk, set, rst;
```

```
output reg q;
```

```
always @(posedge clk)
```

```
if (rst)
```

```
q <= 0;
```

```
else if (set)
```

```
q <= 1;
```

```
else
```

```
q <= d; //IF WE DONT MENTION THIS ELSE CONDITION< WE WILL ENCOUNTER A LATCH
```

```
endmodule
```

### TESTBENCH: -

```
module dff_tb;
```

```
reg d, clk, set, rst;
```

```
wire q;
```

```
dff DU(q, d, clk, set, rst);
```

```
always begin
```

```
#2clk=1'b1;
```

```
#2clk=1'b0;
```

```
end
```

```
initial begin
```

```
  @(negedge clk)
```

```
  rst = 1;
```

```
  @(negedge clk)
```

```
  rst = 0;
```

```
  #5;
```

```
  @(posedge clk)d = 1;
```

```
  @(posedge clk)d = 0;
```

```
  @(posedge clk)d = 0;
```

```
  @(posedge clk)d = 1;
```

```
#50 $finish;
```

```
end
```

```
initial
```

```
  $monitor("for input d:%b, output is:%b",d,q);
```

```
initial
```

```
begin
```

```
  $dumpfile("dff.vcd");
```

```
$dumpvars();
```

```
end
```

```
endmodule
```

## **OUTPUT: -**

Time resolution is 1 ps

for input d:x, output is:x


for input d:1, output is:1

for input d:0, output is:0

for input d:1, output is:1

\$finish called at time : 76 ns



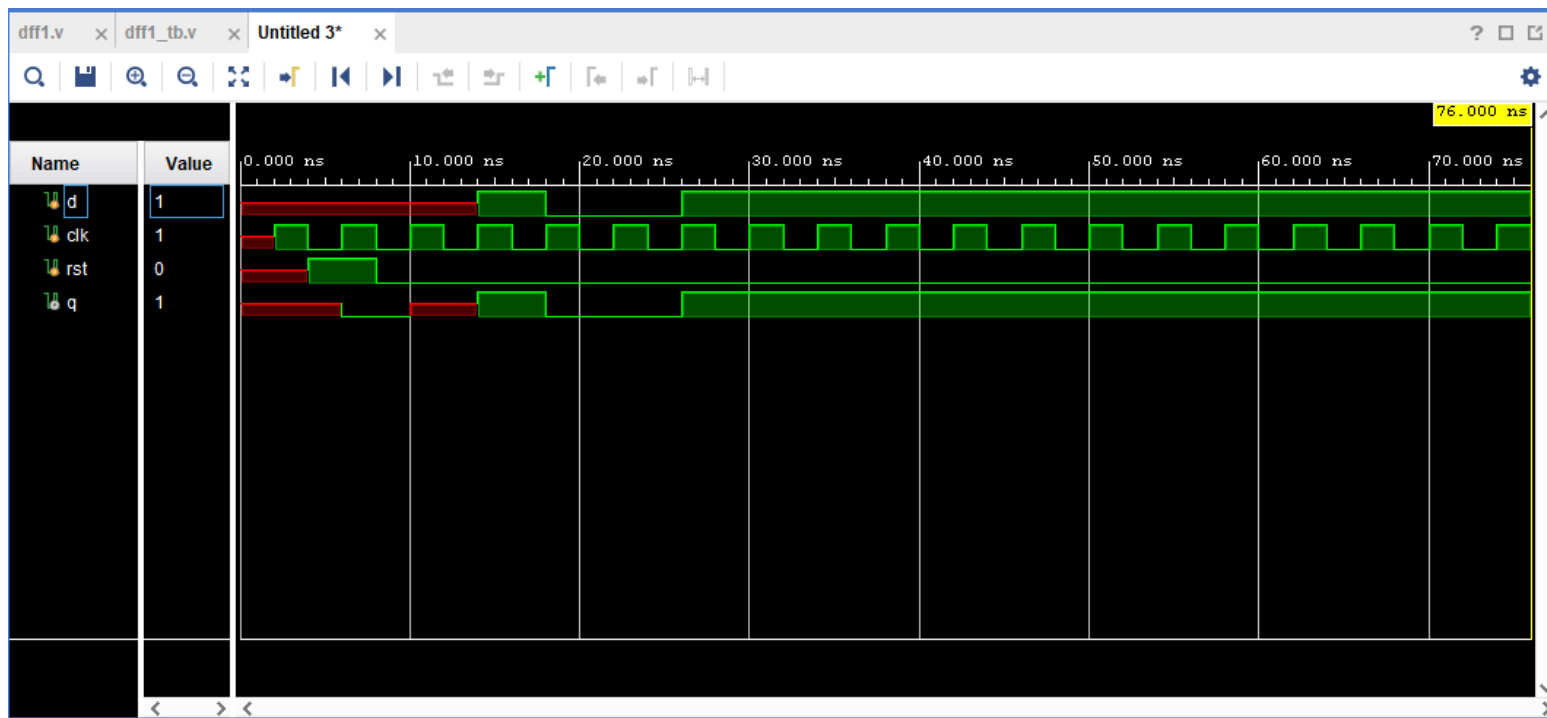

## [5]. Race Condition.

### #1\_READ-WRITE RACE.

```
module test;
```

```
reg a,b,clk;
```

```
always begin
```

```
    #3clk = 1'b1;
```

```
    #3clk = ~clk;
```

```
end
```

```
always @(posedge clk) begin
```

```
    a <= 1;
```

```
end
```

```
always @(posedge clk) begin
```

```
    b <= a;
```

```
    #50 $finish;
```

```
end
```

```
endmodule
```

[ If we didn't opt for non-blocking assignments for 'a' and 'b', one always block value is assigned to 'a' while simultaneously its value is assigned to 'b', which means 'a' is writing and read parallel. This type of race condition is solved by using nonblocking assignment for both 'a' and 'b'.]

### #2\_WRITE-WRITE RACE.

```

module test;

reg a,b,clk;

always begin

    #3clk = 1'b1;

    #3clk = ~clk;

end

always @(posedge clk)

a = 1;

always @(posedge clk)

a = 5;

    #50 $finish;

end

endmodule

```

[In this case, we can see that one block is updating value of ‘a’ while another one is doing the same thing with a different value. So there is an ambiguity as to which ‘always’ block should execute first. This is nondeterministic and it completely depends on the simulator algorithm.]

```

-----#####-----
-----#####-----

```

## FSM Assignment

### Snippet #1: - (SEQUENCE DETECTOR(1011) FSM CODING STYLE #1)

RTL: -

```

module sequence(clk, reset, din, dout);

```

```

input clk, reset, din;

```

```

output dout;

```

```

parameter IDLE = 5'b00001,

```

```

    S1 = 5'b00010,

```

```

    S2 = 5'b00100,

```

```

    S3 = 5'b01000,

```

```

    S4 = 5'b10000;

```

```

reg [4:0]next_state, state;

```

```
//PRESENT STATE LOGIC (SEQUENTIAL)
```

```
always@(posedge clk) begin
```

```
if(reset)
```

```
state<= IDLE;
```

```
else
```

```
state<= next_state;
```

```
end
```

```
always@(*) begin
```

```
case(state)
```

```
IDLE: begin
```

```
    if(din==1)
```

```
        next_state = S1;
```

```
    else
```

```
        next_state = IDLE;
```

```
end
```

```
S1: begin
```

```
    if(din==0)
```

```
        next_state = S2;
```

```
    else
```

```
        next_state = S1;
```

```
end
```

```
S2: begin
```

```
    if(din==1)
```

```
        next_state = S3;
```

```
    else
```

```
        next_state = IDLE;
```

```
end
```

```
S3: begin
    if(din==1)
        next_state = S4;
    else
        next_state = S2;
    end
```

```
S4: begin
    if(din==1)
        next_state = S1;
    else
        next_state = S2;
    end
```

```
endcase
end
```

```
assign dout = (state==S4) ? 1:0;
```

```
endmodule
```

### **TESTBENCH: -**

```
module sequence_tb;
```

```
reg clk, reset, din;
```

```
wire dout;
```

```
sequence DUT(clk, reset, din, dout);
```

```
always begin
```

```
#2clk = 1'b1;
```

```
#2 clk = ~clk;
```

```
end
```

```
initial begin
```

```

@(negedge clk)
reset = 1'b1;

@(negedge clk)
reset = 1'b0;

    @(posedge clk) din <= 1;
    @(posedge clk) din <= 0;
    @(posedge clk) din <= 1;
    @(posedge clk) din <= 1;           // Sequence is detected.
    @(posedge clk) din <= 0;
    @(posedge clk) din <= 0;
    @(posedge clk) din <= 1;
    @(posedge clk) din <= 1;
    @(posedge clk) din <= 0;
    @(posedge clk) din <= 1;
    @(posedge clk) din <= 1;

#100 $finish;

end

initial

$monitor($time,"For input:%0b, Output is %0b",din, dout);

endmodule

```

### **Output Snippet #1:-**

Time resolution is 1 ps

```

0For input:x, Output is x
6For input:x, Output is 0
10For input:1, Output is 0
14For input:0, Output is 0
18For input:1, Output is 0
26For input:0, Output is 1
30For input:0, Output is 0
34For input:1, Output is 0
42For input:0, Output is 0


```

46For input:1, Output is 0

54For input:1, Output is 1

58For input:1, Output is 0

\$finish called at time : 150 ns

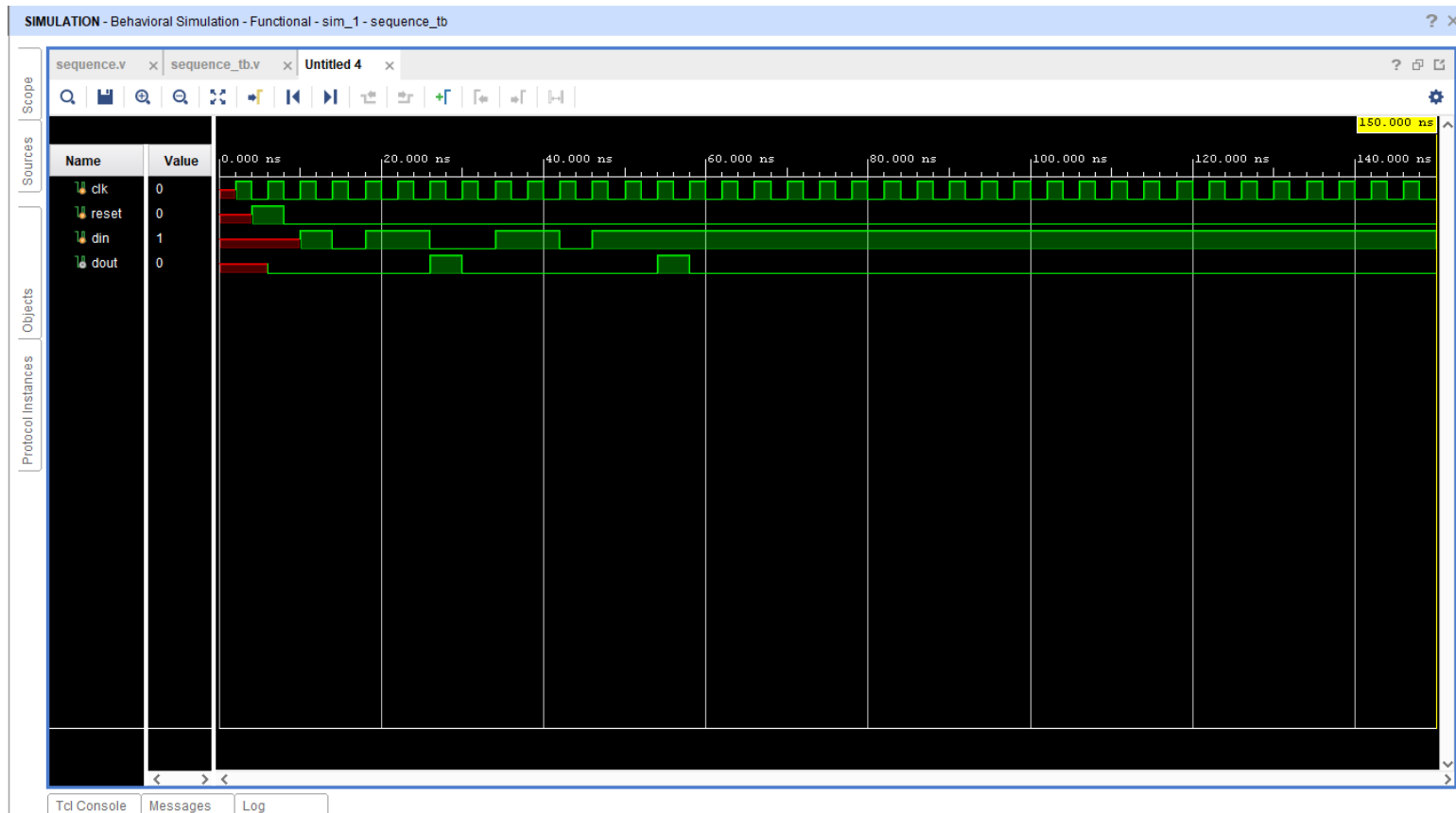

-----#####-----

## **Snippet #2: - (SEQUENCE DETECTOR(0101/1011) FSM CODING STYLE #2)**

**RTL: -**

```
module sequence(clk , reset, din, dout);
```

```
input clk, reset, din;
```

```
output reg dout;
```

```
parameter IDLE = 4'b0000,
```

```
    S0 = 4'b0001,
```

```
    S1 = 4'b0010,
```

```
    S2 = 4'b0011,
```

```
    S3 = 4'b0100,
```

```
    S4 = 4'b0101,
```

```
    S5 = 4'b0110,
```

```
    S6 = 4'b0111,
```

```
    S7 = 4'b1000;
```

```
reg [3:0]next_state, state;
```

```
always@(posedge clk) begin
```

```
if(reset)
```

```
state<= IDLE;
```

```
else
```

```
state<= next_state;
```

```
end
```

```
always@(*) begin
```

```
case(state)
```

```
IDLE: begin
```

```
    dout = 0;
```

```
    if(din==0)
```

```
        next_state = S0;
```

```
    else
```

```
        next_state = S4;
```

```
end
```

```
S0: begin
```

```
    dout = 0;
```

```
    if(din==1)
```

```
        next_state = S1;
```

```
    else
```

```
        next_state = S0;
```

```
end
```

```
S1: begin
```

```
    if(din==0)
```

```
        next_state = S2;
```

```
    else
```

```
        next_state = S4;
```

```
end
```

S2: begin

```
dout = 0;  
if(din==1)  
    next_state = S3;  
else  
    next_state = S0;  
end
```

S3: begin

```
dout = 1;  
if(din==1)  
    next_state = S7;  
else  
    next_state = S5;  
end
```

S4: begin

```
dout = 0;  
if(din==0)  
    next_state = S5;  
else  
    next_state = S4;  
end
```

S5: begin

```
dout = 0;  
if(din==1)  
    next_state = S6;  
else  
    next_state = S0;  
end
```

S6: begin

```
dout = 0;
```



```
    if(din==1)
        next_state = S7;
    else
        next_state = S2;
    end
```

```
S7: begin
    dout = 1;
    if(din==1)
        next_state = S4;
    else
        next_state = S5;
    end
```

```
endcase
```

```
end
```

```
endmodule
```

### **TESTBENCH: -**

```
module sequence_tb;
    reg clk, reset, din;
    wire dout;
    sequence DUT(clk, reset, din, dout);
    always begin
        #2clk = 1'b1;
        #2 clk = ~clk;
    end
```

```
    initial begin
        @(negedge clk)
        reset = 1'b1;
        @(negedge clk)
```

```
reset = 1'b0;
```

```
@(posedge clk) din <= 0;
@(posedge clk) din <= 1;
@(posedge clk) din <= 0;
@(posedge clk) din <= 1;           // Sequence is detected.
@(posedge clk) din <= 1;
@(posedge clk) din <= 0;
@(posedge clk) din <= 1;
@(posedge clk) din <= 1;
@(posedge clk) din <= 1;
@(posedge clk) din <= 0;
@(posedge clk) din <= 1;
@(posedge clk) din <= 0;
```

```
#100 $finish;
```

```
end
```

```
initial
```

```
$monitor($time,"For input:%0b, Output is %0b",din, dout);
```

```
endmodule
```

## **Output Snippet #2:-**

Time resolution is 1 ps

0For input:x, Output is x

6For input:x, Output is 0

10For input:0, Output is 0

14For input:1, Output is 0

18For input:0, Output is 0

22For input:1, Output is 0

26For input:1, Output is 1

30For input:0, Output is 1

34For input:1, Output is 0


42For input:1, Output is 1

46For input:0, Output is 0

50For input:1, Output is 0

54For input:0, Output is 0

\$finish called at time : 154 ns

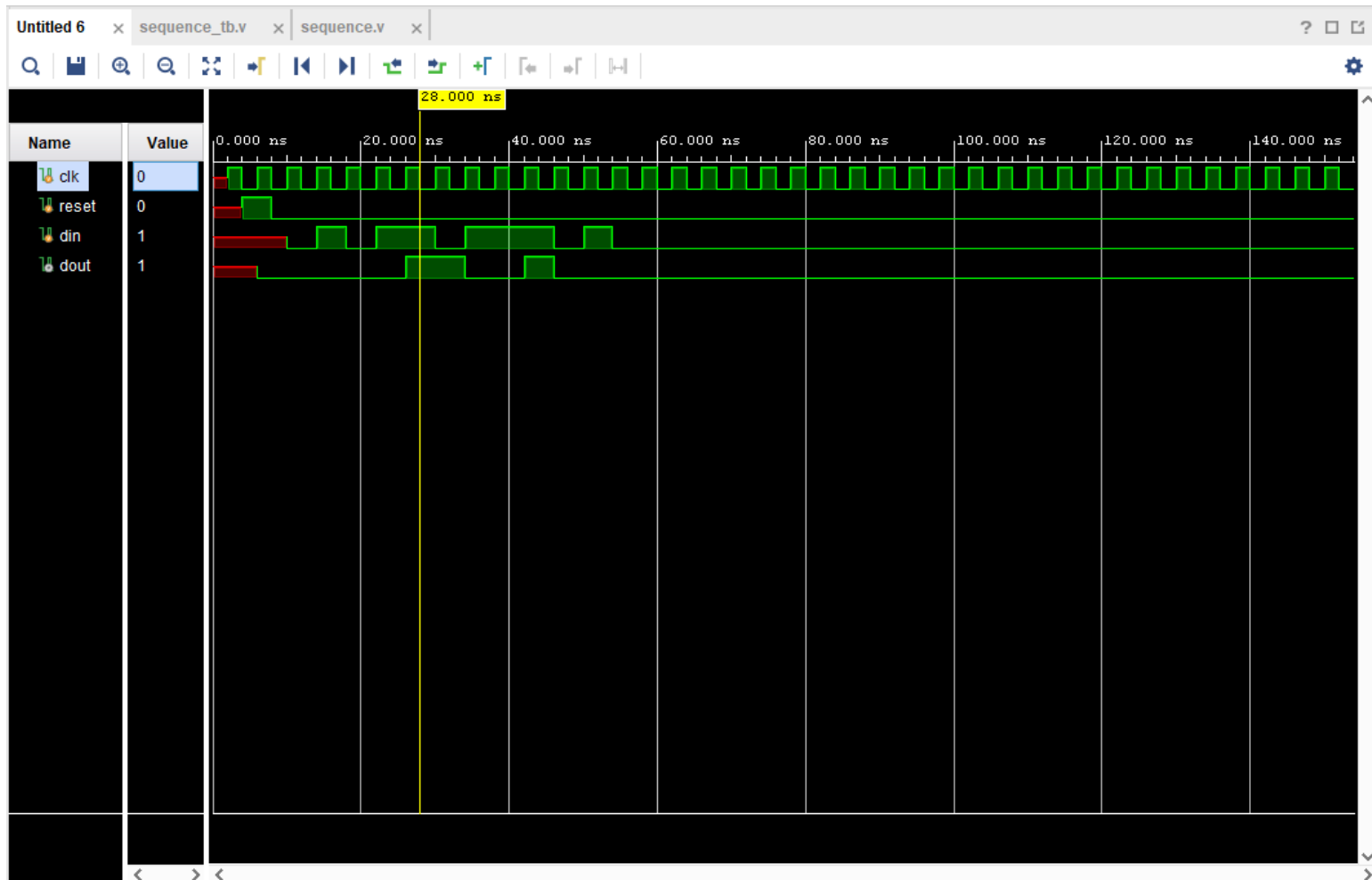

-----#####-----

You are hired by Pepsi to design their next generation Pepsi (Generation Next) machine, the reason being that Pepsi is going to drop the price of their product to a quarter( $1/4^{\text{th}}$  of a dollar = 25 cents). The new machine will accept the industry standard nickel=5 cents, dime=10 cents and quarter=25 cents . Design a totally synchronous FSM and write the RTL code for the same. Assume the only inputs to the system are the type of change put in (nickel, dime, or quarter). Your outputs will be two change amount(Change 1 & Change 2), and a Pepsi release signal that goes high when enough change has been put in.

Example: If the total = 40 cents then Output : Pepsi = 1, Change 1 = 10 & Change 2 = 5 (Order of change can be interchangeable)

# FSM for the vending machine:-


IP = 5, 10, 25

Pepsi delivered @ 25

Suyash Chavan

Change 1:  
(10/5)

Change 2:  
(10/5)

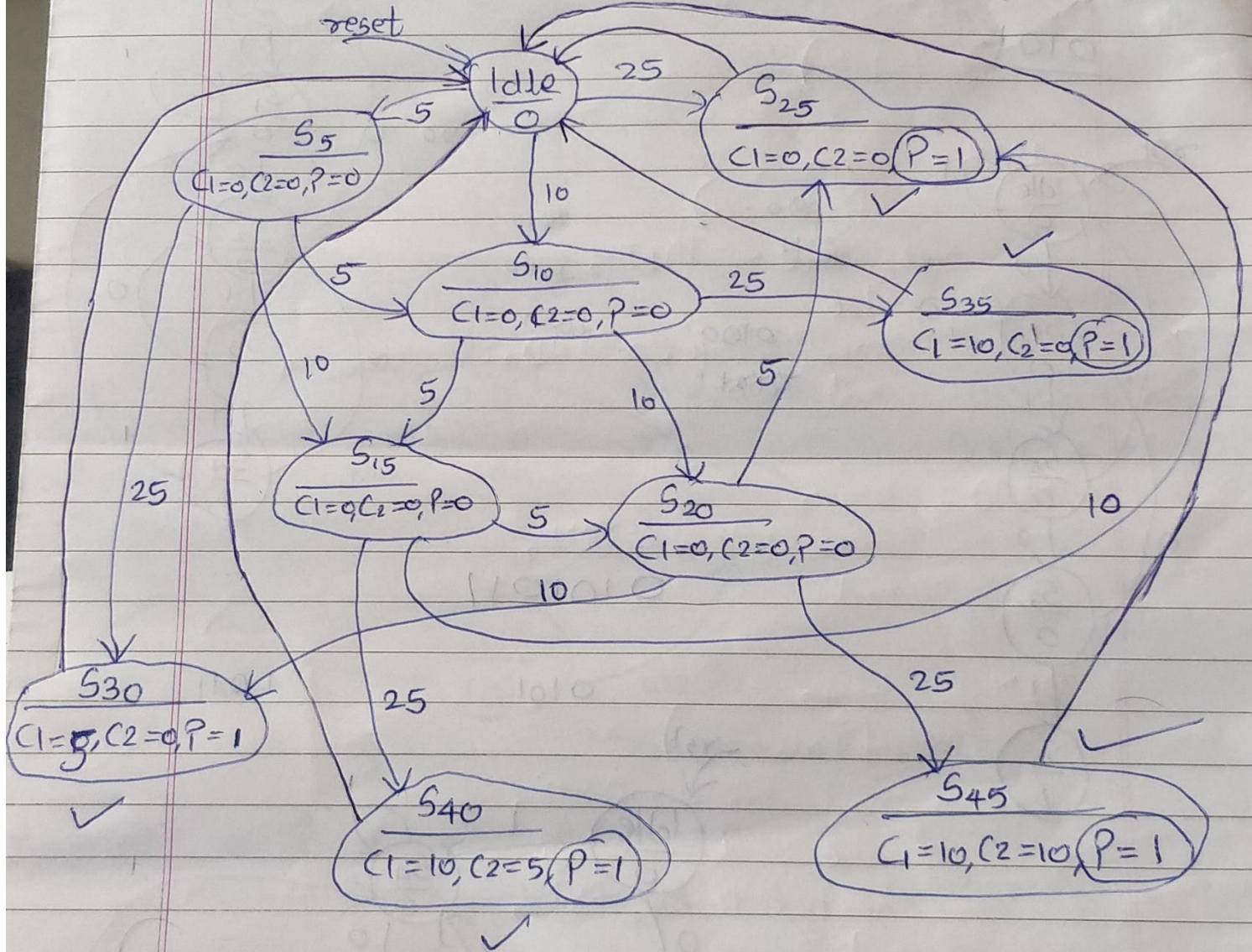

din(5) : 2'b 00  
din(10) : 2'b 01  
din(25) : 2'b 10

**RTL: -**

```
module vending_fsm(din,clock,reset,p,c1,c2);
```

```
    input [1:0]din;
```

```
    input clock,reset;
```

```
    output reg p;
```

```
    output reg[3:0]c1,c2;
```

```
    parameter                                IDLE=4'b0000,
                                             S5=4'b0001,
                                             S10=4'b0010,
                                             S15=4'b0011,
                                             S20=4'b0100,
                                             S25=4'b0101,
                                             S30=4'b0110,
                                             S35=4'b0111,
                                             S40=4'b1000,
                                             S45=4'b1001;
```

```
    reg [3:0] next_state, state;
```

```
    always@(posedge clock)begin
```

```
        if(reset)
```

```
            state<=IDLE;
```

```
        else
```

```
            state<=next_state;
```

```
        end
```

```
    always@(*)begin
```

```
        case (state)
```

```
            IDLE:
```

```
                if(din==2'b00)
```

```
                    next_state=S5;
```

```
                else if(din==2'b01)
```

```
                    next_state=S10;
```

```
        else if(din==2'b10)
next_state=S25;
        else
next_state=IDLE;
```

S5:

```
    if (din==2'b00)

        next_state=S10;
        else if(din==2'b01)

next_state=S15;

        else if(din==2'b10)
            next_state=S30;

    else
next_state=IDLE;
```

S10:

```
    if (din==2'b00)
next_state=S15;

        else if(din==2'b01)

next_state=S20;

        else if(din==2'b10)
            next_state=S35;

    else
next_state=IDLE;
```

S15:

```
    if (din==2'b00)
next_state=S20;

        else if(din==2'b01)

next_state=S25;

        else if(din==2'b10)
next_state=S40;
```

```
else
next_state=IDLE;
```

S20:

```
if (din==2'b00)
next_state=S25;

else if(din==2'b01)

next_state=S30;

else if(din==2'b10)
next_state=S45;
```

```
else
next_state=IDLE;
```

S25 : next\_state=IDLE;

S30 : next\_state=IDLE;

S35 : next\_state=IDLE;

S40 : next\_state=IDLE;

S45 : next\_state=IDLE;

default : next\_state=IDLE;

endcase

end

always@(\*)

begin

p=1'b0; c1=4'd0; c2=4'd0;

case (state)

IDLE :begin

p=1'b0; c1=4'd0; c2=4'd0;

end

```
S5 : begin
    p=1'b0; c1=4'd0; c2=4'd0;
    end

S10 : begin
    p=1'b0; c1=4'd0; c2=4'd0;
    end

S15 : begin
    p=1'b0; c1=4'd0; c2=4'd0;
    end

S20 : begin
    p=2'b0; c1=4'd0; c2=4'd0;
    end

S25 : begin
    p=1'b1; c1=4'd0; c2=4'd0;
    end

S30 : begin
    p=1'b1; c1=4'd5; c2=4'd0;
    end

S35 : begin
    p=1'b1; c1=4'd10; c2=4'd0;
    end

S40 : begin
    p=1'b1; c1=4'd10; c2=4'd5;
    end

S45 : begin
    p=1'b1; c1=4'd10; c2=4'd10;
    end

default : begin
    p=1'b0; c1=4'd0; c2=4'd0;
    end

endcase
```

end

endmodule

**TESTBENCH: -**



```

module vending_fsm_tb;

reg [1:0]din;

reg clock,reset;

wire p;

wire[3:0]c1,c2;


integer i;


vending_fsm DUT(din,clock,reset,p,c1,c2);


always begin

#2clock = 1'b1;

#2 clock = ~clock;

end


initial begin

@(negedge clock)

reset = 1'b1;

@(negedge clock)

reset = 1'b0;


din = 2'b00;

#1;

din = 2'b01;

#1;

din = 2'b00;

#1;

din = 2'b00;

#5;

din = 2'b10;


#20 $finish;

end

```

initial

```
$monitor($time,"For input coins:%b, Pepsi delivered:%b",din, p);
```


endmodule

**Output: -**

Time resolution is 1 ps

- 0For input coins:xx, Pepsi delivered:x
- 6For input coins:xx, Pepsi delivered:0
- 8For input coins:00, Pepsi delivered:0
- 9For input coins:01, Pepsi delivered:0
- 10For input coins:00, Pepsi delivered:0
- 16For input coins:10, Pepsi delivered:0
- 18For input coins:10, Pepsi delivered:1
- 22For input coins:10, Pepsi delivered:0
- 26For input coins:10, Pepsi delivered:1
- 30For input coins:10, Pepsi delivered:0
- 34For input coins:10, Pepsi delivered:1

\$finish called at time : 36 ns

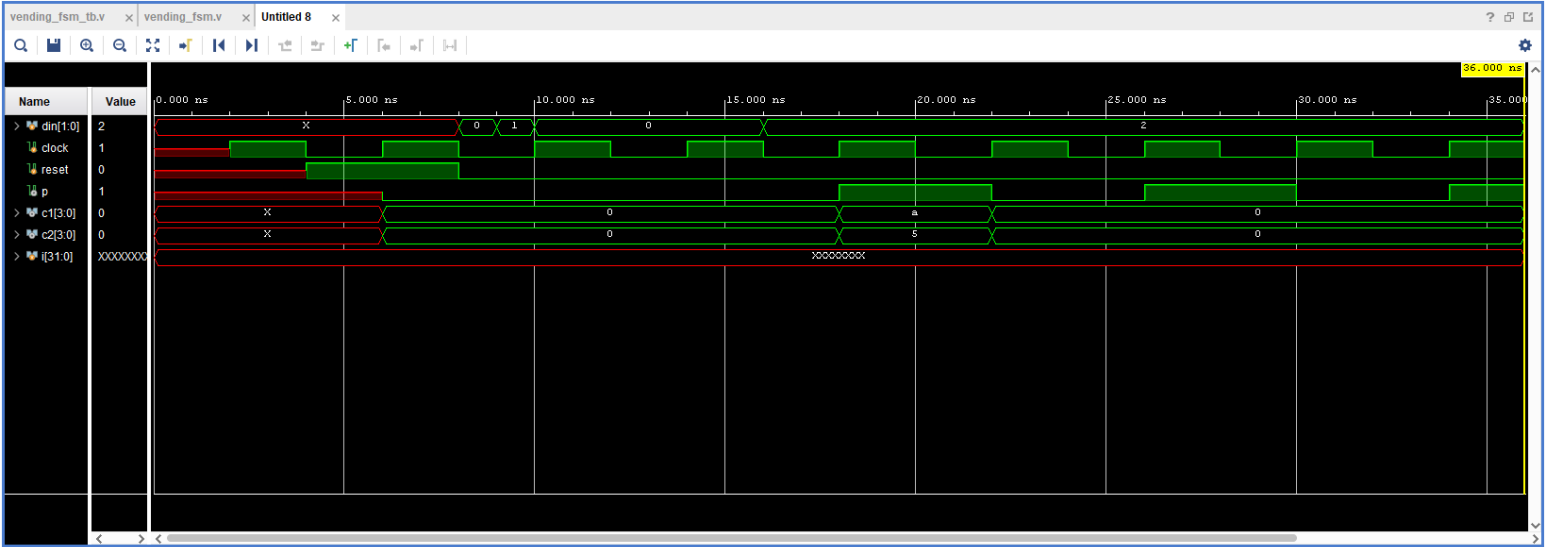

-----#####-----

#### **Snippet #4: - (SEQUENCE DETECTOR (0110) FSM CODING STYLE #3)**

**RTL: -**

```
module mealy_fsm(clk,reset,din,dout);
```

```
input clk,reset,din;
```

```
output reg dout;
```

```
parameter IDLE=3'b001,
```

```
        S1=3'b010,
```

```
        S2=3'b011,
```

```
        S3=3'b100;
```

```
reg[2:0]next_state, state;
```

```
always@(posedge clk) begin
```

```
if(reset)
```

```
state<=IDLE;
```

```
else
```

```
state<=next_state;
```

```
end
```

```
always@(*) begin
```

```
    next_state=IDLE;
```

```
    case(state)
```

```
        IDLE: begin
```

```
            if(din==0)
```

```
                next_state=S1;
```

```
            else
```

```
                next_state=IDLE;
```

end

S1: begin

if(din==1)

next\_state=S2;

else

next\_state=S1;

end

S2: begin

if(din==1)

next\_state=S3;

else

next\_state=S1;

end

S3: begin

if(din==0)

next\_state=S1;

else

next\_state=IDLE;

end

endcase

end

always@(posedge clk) begin

if(reset)

dout<=0;

else

begin

dout<=0;

```
        case(state)

            IDLE: dout<=0;

            S1:  dout<=0;

            S2:  dout<=0;

            S3:  dout<=1;


        endcase

    end

end

endmodule
```

**TESTBENCH: -**

```
module mealy_fsm_tb();

    reg din,

        clk,

        reset;


    wire dout;


    parameter CYCLE=10;


    mealy_fsm DUT(.din(din),

        .clk(clk),

        .reset(reset),

        .dout(dout));


    always

    begin

        #(CYCLE/2);

        clk=1'b0;

        #(CYCLE/2);

        clk=~clk;
```

```
end
```

```
task initialize;
```

```
begin
```

```
din=1'b0;
```

```
reset=1'b0;
```

```
end
```

```
endtask
```

```
task delay(input integer i);
```

```
begin
```

```
    #i;
```

```
end
```

```
endtask
```

```
task RESET;
```

```
begin
```

```
@(negedge clk)
```

```
reset= 1'b1;
```

```
@(negedge clk)
```

```
reset=1'b0;
```

```
end
```

```
endtask
```

```
task stimulus(input i);
```

```
begin
```

```
@(negedge clk)
```

```
din=i;
```

```
end
```

```
endtask
```

```
initial $monitor(" Reset=%b, state=%d, Din=%b, Output Dout=%b",  
                reset,DUT.state,din,dout);
```

```
initial  
begin  
    initialize;  
    RESET;  
    stimulus(0);  
    delay(10);  
  
    stimulus(1);  
    delay(10);  
  
    stimulus(1);  
    delay(10);  
  
    stimulus(0);  
    delay(10);  
  
    stimulus(1);  
    delay(10);  
  
    stimulus(1);  
    delay(10);  
  
    stimulus(0);  
delay(10);  
  
    $finish;  
end
```

```
initial  
begin
```

```
$dumpfile("seq.vcd");


$dumpvars();

end

endmodule
```

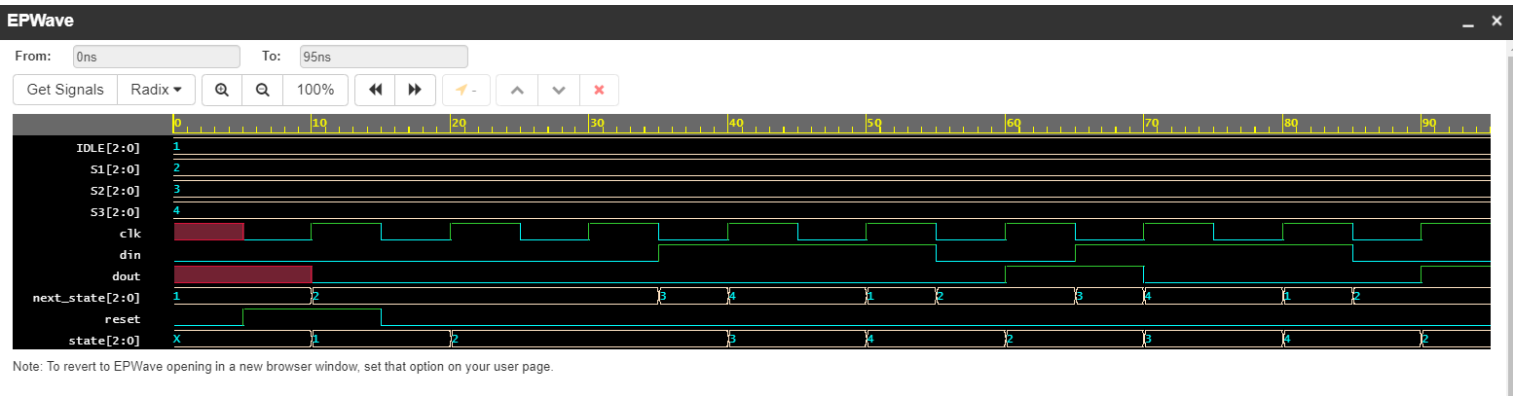**Output: -**

```
# KERNEL: Reset=0, state=x, Din=0, Output Dout=x
# KERNEL: Reset=1, state=x, Din=0, Output Dout=x
# KERNEL: Reset=1, state=1, Din=0, Output Dout=0
# KERNEL: Reset=0, state=1, Din=0, Output Dout=0
# KERNEL: Reset=0, state=2, Din=0, Output Dout=0
# KERNEL: Reset=0, state=2, Din=1, Output Dout=0
# KERNEL: Reset=0, state=3, Din=1, Output Dout=0
# KERNEL: Reset=0, state=4, Din=1, Output Dout=0
# KERNEL: Reset=0, state=4, Din=0, Output Dout=0
# KERNEL: Reset=0, state=2, Din=0, Output Dout=1
# KERNEL: Reset=0, state=2, Din=1, Output Dout=1
# KERNEL: Reset=0, state=3, Din=1, Output Dout=0
# KERNEL: Reset=0, state=4, Din=1, Output Dout=0
# KERNEL: Reset=0, state=4, Din=0, Output Dout=0
# KERNEL: Reset=0, state=2, Din=0, Output Dout=1
# RUNTIME: Info: RUNTIME_0068 testbench.sv (144): $finish called.
# KERNEL: Time: 95 ns
```



**Snippet #5: - (SEQUENCE DETECTOR (1011) FSM CODING STYLE #2)**

**RTL: -**

```
module sequence_detector(clock,reset,din,dout);

input clock;

input reset;

input din;

output reg dout;

parameter S0=3'b000,
```



S1=3'b001,

S2=3'b011,

S3=3'b010,

S4=3'b110;

reg [2:0] current\_state, next\_state;

always @(posedge clock, posedge reset)

begin

if(reset==1)

current\_state <= S0;

else

current\_state <= next\_state;

end

always @(current\_state,din)

begin

case(current\_state)

S0:begin

if(din==1)

next\_state = S1;

else

next\_state = S0;

end

S1:begin

if(din==0)

next\_state = S2;

else

next\_state = S1;

end

S2:begin

if(din==0)

next\_state = S0;

else

next\_state = S3;

```
end
S3:begin
  if(din==0)
    next_state = S2;
  else
    next_state = S4;
  end
end
S4:begin
  if(din==0)
    next_state = S2;
  else
    next_state = S1;
  end
end
default:next_state = S0;
endcase
end
```

```
always @(current_state)
begin
  case(current_state)
S0:  dout = 0;
S1:  dout = 0;
S2:  dout = 0;
S3:  dout = 0;
S4:  dout = 1;
default:  dout = 0;
  endcase
end
endmodule
```

#### **TESTBENCH: -**

```
module sequence_detector_tb;

  reg din;

  reg clock;
```

```
reg reset;
```

```
wire dout;
```

```
sequence_detector DUT(clock,reset,din,dout);
```

```
always begin
```

```
#5clock = 1;
```

```
#5clock = ~clock;
```

```
end
```

```
initial begin
```

```
    din = 0;
```

```
    reset = 1;
```

```
    #5;
```

```
        reset = 0;
```

```
    #10;
```

```
    din = 1;
```

```
    #10;
```

```
    din = 0;
```

```
    #10;
```

```
    din = 1;
```

```
    #20;
```

```
    din = 1;
```

```
    #20;
```

```
    din = 0;
```

```
    #20;
```

```
    din = 0;
```

```
    #5 $finish;
```

```
end
```

```
initial
```

```
    $monitor($time,"For the input:%b, detector output is %b", din, dout);
```

```
endmodule
```

## Output: -

0For the input:0, detector output is 0

15For the input:1, detector output is 0

25For the input:0, detector output is 0

35For the input:1, detector output is 0

45For the input:1, detector output is 1

55For the input:1, detector output is 0

75For the input:0, detector output is 0

\$finish called at time : 100 ns

